

BWW Ex 11.7

I

3-fasig diodlikriktare med RL-last 10Ω , 50mH
Nätspänning 415V , 50Hz

i) Medelspänning och ström

Medelspänningen fås genom att integrera

$$\hat{U}_{LL} \cos(\omega t) \text{ över } -\frac{\pi}{6} \leq \omega t \leq \frac{\pi}{6}$$

$$\begin{aligned} V_{dc} &= \frac{1}{T/6} \int_{T/6} \hat{U}_{LL} \cos(\omega t) dt = \frac{1}{T/6} \int_{T/6} \hat{U}_{LL} \cos(\omega t) dt \cdot \omega \cdot \frac{1}{\omega} = \\ &= \frac{1}{\omega T/6} \int_{-\pi/6}^{\pi/6} \hat{U}_{LL} \cos(\omega t) d(\omega t) = \frac{6}{\omega T} \left[\hat{U}_{LL} \sin(\omega t) \right]_{-\pi/6}^{\pi/6} = \{ \omega T = 2\pi \} = \\ &= \frac{\hat{U}_{LL} \cdot 6}{2\pi} \left(\sin \frac{\pi}{6} - \sin \left(-\frac{\pi}{6} \right) \right) = \frac{\hat{U}_{LL} \cdot 6}{2\pi} \underbrace{2 \sin \frac{\pi}{6}}_{1/2} = \\ &= \frac{\hat{U}_{LL} \cdot 6}{2\pi} = \frac{3 \cdot \sqrt{2} \cdot U_{LL}}{\pi} = 1,35 \cdot U_{LL} = \underline{\underline{560,45\text{V}}} \end{aligned}$$

Medelspänningen över d är noll. Alltså ligger hela medelspänningen över R . $\Rightarrow I_{\text{LOAD}} = \frac{V_{dc}}{R_{\text{LOAD}}} = \underline{\underline{56,05\text{A}}}$

ii) RMS-spänningen fås som: $V_{\text{RMS}} = \sqrt{\frac{1}{T} \int U^2(t) dt}$

Alltså måste $U_{LL}^2(t)$ integreras

$$\begin{aligned} U_{LL}^2(t) &= (\hat{U}_{LL} \cos(\omega t))^2 = \hat{U}_{LL}^2 \cdot \cos^2(\omega t) = \{ \cos 2\alpha = 2\cos^2\alpha - 1 \} \\ &= \frac{\hat{U}_{LL}^2}{2} (1 + \cos(2\omega t)) \end{aligned}$$

$$\begin{aligned} V_{dc, \text{RMS}} &= \sqrt{\frac{1}{T/6} \int_{T/6} \frac{\hat{U}_{LL}^2}{2} (1 + \cos(2\omega t)) dt} = \\ &= \sqrt{\frac{1}{\omega T/6} \int_{-\pi/6}^{\pi/6} \frac{\hat{U}_{LL}^2}{2} (1 + \cos(2\omega t)) d(\omega t)} = \end{aligned}$$

$$= \sqrt{\frac{3 \hat{U}_{LL}^2}{\omega T} \left[\omega t + \frac{1}{2} \sin(2\omega t) \right]_{-\pi/6}^{\pi/6}} =$$

$$= \sqrt{\frac{3 \hat{U}_{LL}^2}{\omega T} \left(\frac{\pi}{6} - \left(-\frac{\pi}{6}\right) + \frac{1}{2} \left(\sin \frac{\pi}{3} - \sin \left(-\frac{\pi}{3}\right) \right) \right) =$$

$$= \sqrt{\frac{3 \hat{U}_{LL}^2}{2\pi} \left(\frac{\pi}{3} + \sin \frac{\pi}{3} \right)} = \sqrt{\frac{3 \hat{U}_{LL}^2}{2\pi} \left(\frac{\pi}{3} + \frac{\sqrt{3}}{2} \right)} =$$

$$= \hat{U}_{LL} \sqrt{\frac{1}{2} + \frac{3\sqrt{3}}{4\pi}} = U_{LL\text{RMS}} \cdot \sqrt{2} \sqrt{\frac{1}{2} + \frac{3\sqrt{3}}{4\pi}} =$$

$$= U_{LL\text{RMS}} \sqrt{1 + \frac{3\sqrt{3}}{2\pi}} = U_{LL\text{RMS}} \cdot 1,35166 = \underline{\underline{560,94\text{V}}}$$

$$V_{dc\text{RMS}} = \sqrt{V_{ac\text{RMS}}^2 + V_{dc\text{AVG}}^2} \Rightarrow$$

$$V_{ac\text{RMS}} = \sqrt{V_{dc\text{RMS}}^2 - V_{dc\text{AVG}}^2} = \sqrt{560,94^2 - 560,45^2} = \underline{\underline{23,45\text{V}}}$$

U. Förlusterna i en diöd kan beräknas mha.
medelström och RMS-ström enligt:

$$P_D = \frac{1}{3} (V_{T0} \cdot \bar{I}_0 + R_T \cdot I_0^2) \leftarrow \text{Detta kommer att visas}$$

\leftarrow varje diöd leder senare i kursen!
bara 1/3 av tiden

$$V_{T0} \cdot \frac{\bar{I}_0}{3} + R_T \left(\frac{\bar{I}_0}{\sqrt{3}} \right)^2 = V_{T0} \cdot I_{D\text{AVG}} + R_T \cdot I_{D\text{RMS}}^2 \Rightarrow$$

$$I_{D\text{AVG}} = \frac{\bar{I}_0}{3} = \frac{56,045}{3} = \underline{\underline{18,7\text{A}}}$$

$$I_{D\text{RMS}} = \frac{\bar{I}_0}{\sqrt{3}} = \frac{56,045}{\sqrt{3}} = \underline{\underline{32,4\text{A}}} \quad (\text{Fel i boken})$$