

$T = \text{TILL: } V_1 = V_{dc} \Rightarrow V_2 = \frac{N_2}{N_1} \cdot V_1 = \frac{N_2}{N_1} V_{dc}$

$L \frac{di_2}{dt} = V_2 - V_0 \Rightarrow \Delta i_2 = \frac{N_2/N_1 V_{dc} - V_0}{L} t_T$


$T = \text{FRÅN: } -L \frac{di_2}{dt} = V_0 \Rightarrow |\Delta i_2| = \frac{V_0}{L} \cdot t_D$
 ↑ negativ derivata

LIKHET: Antag ansluten drift på utgången, alltså kontinuerlig ström i L:

$(N_2/N_1 V_{dc} - V_0) \cdot \delta_T T = V_0 (1 - \delta_T) T$

$\bar{i}_c \quad V_0 = \frac{N_2}{N_1} \cdot V_{dc} \cdot \delta = \frac{1}{1} \cdot 96 \cdot 0,4 = 38,4V$

Spänningsrippel i kondensatorn

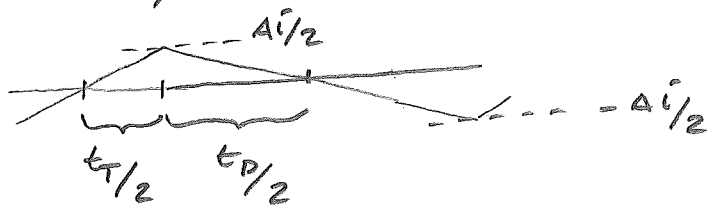

Räkna bara på intervallet när $\bar{i}_c > 0$

$\bar{i}_c = C \frac{dV_c}{dt} \Rightarrow \Delta V_c = \frac{1}{C} \int \bar{i}_c dt =$

$= \frac{1}{C} \left(\int_0^{t_T/2} \frac{\Delta i_c/2}{t_T/2} \cdot t dt + \int_0^{t_D/2} \left[\frac{\Delta i_c}{2} - \frac{\Delta i_c/2}{t_D/2} \cdot t \right] dt \right) =$

$= \frac{1}{C} \left(\left[\frac{\Delta i_c}{t_T} \cdot \frac{t^2}{2} \right]_0^{t_T/2} + \left[\frac{\Delta i_c}{2} \cdot t - \frac{\Delta i_c}{t_D} \cdot \frac{t^2}{2} \right]_0^{t_D/2} \right) =$

$$= \frac{1}{C} \left(\frac{\Delta i}{8} t_T + \frac{\Delta i}{4} \cdot t_D - \frac{\Delta i}{8} t_D \right) =$$

$$= \frac{1}{C} \left(\frac{\Delta i}{8} t_T + \frac{\Delta i}{8} t_D \right) = \{t_D + t_T = T\} = \frac{1}{8} \frac{\Delta i T}{C}$$

$$\Delta i = \Delta i_2 = \{ \text{enl. "T=ERÅN"} \} = \frac{V_0}{L} \cdot t_D = \frac{V_0}{L} (1-\delta) T$$

$$\Delta U_c = \frac{1}{8} \frac{V_0}{LC} (1-\delta) T^2 = \frac{1}{8} \frac{38,4}{250 \mu\text{H} \cdot 220 \mu\text{F}} (1-0,4) \cdot \left(\frac{1}{40 \text{kHz}} \right)^2 =$$

$$= 32,7 \text{ mV}$$

$$\text{ii)} \quad \bar{I}_0 = \frac{V_0}{R_{\text{LOAD}}} = \frac{38,4}{24} = 1,6 \text{ A}$$

$$\Delta i_2 = \frac{N_2/N_1 \cdot V_{dc} - \bar{V}_0}{L} \cdot \delta T = \frac{1/1 \cdot 96 - 38,4}{250 \cdot 10^{-6}} \cdot 0,4 \frac{1}{40 \text{kHz}} = 2,3 \text{ A}$$

Om ansluten drift: $\bar{I}_0 \geq \frac{\Delta i_2}{2} = \frac{2,3}{2} = 1,15 \text{ Ok}$

iii) I en forward-omvandlare armagnetiseras trafon mellan switchningarna.
Räkna på primärsidan:

$$L_m \frac{\Delta i_m'}{\Delta t} = V_{dc}$$

$$\Delta i_m' = \frac{V_{dc}}{L_m} \Delta t = \frac{V_{dc}}{L_m} \delta \cdot T = \frac{96}{4 \text{mH}} \cdot 0,4 \frac{1}{40 \text{kHz}} = 0,24 \text{ A}$$

iv) I en forward-omvandlare sammanfaller lastströmen och magnetiseringsströmmens toppvärde

$$\hat{i}_T = \hat{i}_L' + \hat{i}_m' = \frac{N_2}{N_1} \hat{i}_L'' + \hat{i}_m' = \frac{N_2}{N_1} \left(\bar{I}_0 + \frac{\Delta i_2}{2} \right) + \hat{i}_m' =$$

$$= \frac{1}{1} \left(1,6 + \frac{2,3}{2} \right) + 0,24 = 2,99 \text{ A}$$