



$$T = \frac{1}{20 \text{ kHz}} = 50 \mu\text{s}$$

i)

$$t_{\text{turn-on}} = t_{ri} + t_{fr} = 100 \text{ ns}$$

$$t_{\text{turn-off}} = t_{fr} + t_{ri} = 200 \text{ ns}$$

$$P_{\text{sw, on}} = \frac{V_{dc} \cdot \bar{I}_d}{2} \cdot t_{\text{turn-on}} \cdot f_{\text{sw}} = \frac{340 \cdot 10}{2} \cdot 100 \cdot 10^{-9} \cdot 20 \cdot 10^3 = 3,4 \text{ W}$$

$$P_{\text{sw, off}} = \frac{V_{dc} \cdot \hat{I}_d}{2} \cdot t_{\text{turn-off}} \cdot f_{\text{sw}} = \frac{340 \cdot 30}{2} \cdot 200 \cdot 10^{-9} \cdot 20 \cdot 10^3 = 20,4 \text{ W}$$

$$P_{\text{sw}} = P_{\text{sw, on}} + P_{\text{sw, off}} = 3,4 + 20,4 = \underline{\underline{23,8 \text{ W}}}$$

ii)

$$P_{\text{cond}} = \frac{1}{T} \int_0^{t_r} \underbrace{R_{\text{DS(on)}}}_{U_{\text{DS}}} \cdot \bar{I}_D(t) \cdot \bar{I}_D(t) dt =$$

$$= \frac{1}{T} \int_0^{t_r} R_{\text{DS(on)}} \cdot \left(\bar{I}_D + \frac{\Delta \bar{I}_D}{t_r} \cdot t \right)^2 dt =$$

$$= \frac{1}{T} \int_0^{t_r} R_{\text{DS(on)}} \left(\bar{I}_D^2 + 2 \bar{I}_D \cdot \frac{\Delta \bar{I}_D}{t_r} \cdot t + \left(\frac{\Delta \bar{I}_D}{t_r} \right)^2 \cdot t^2 \right) dt =$$

$$= \frac{R_{\text{DS(on)}}}{T} \left[\bar{I}_D^2 \cdot t + \bar{I}_D \cdot \frac{\Delta \bar{I}_D}{t_r} t^2 + \left(\frac{\Delta \bar{I}_D}{t_r} \right)^2 \frac{t^3}{3} \right]_0^{t_r} =$$

$$= R_{\text{DS(on)}} \underbrace{\left(\bar{I}_D^2 + \bar{I}_D \cdot \Delta \bar{I}_D + \frac{\Delta \bar{I}_D^2}{3} \right)}_{I_{D, \text{RMS}}^2} \frac{t_r}{T} =$$

$$I_{D, \text{RMS}}^2 \Rightarrow I_{D, \text{RMS}} = 18,03 \text{ A}$$

$$= 0,1 \left(10^2 + 10 \cdot 20 + \frac{20^2}{3} \right) 0,75 = \underline{\underline{32,5 \text{ W}}}$$

iii)

$$T_a = 40^\circ\text{C}$$

$$T_f = P_{\text{Loss}} \cdot R_{th,ja} + T_a =$$

$$= P_{\text{Loss}} (R_{th,jc} + R_{th,ca}) + T_a =$$

$$= (23,8 + 32,5) (0,4 + 0,6) + 40 = 96,3^\circ\text{C}$$