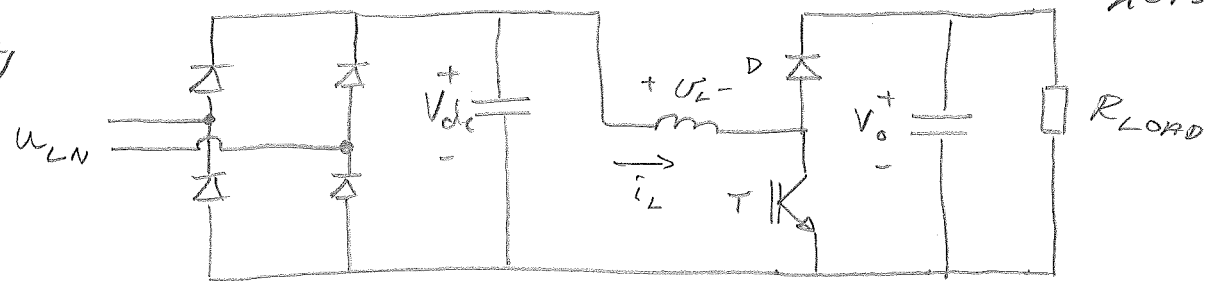


1. a)



b)

$$V_{dc} = \frac{1}{T/2} \int_{T/2}^{\pi} \hat{u}_{LN} \sin(\omega t) dt = \frac{2}{\omega T} \int_0^{\pi} \hat{u}_{LN} \sin(\omega t) d(\omega t) =$$

$$= \frac{2 \hat{u}_{LN}}{2\pi} [-\cos(\omega t)]_0^{\pi} = \frac{2 \sqrt{2} U_{LN,RMS}}{2\pi} (-(-1) + 1) =$$

$$= \frac{2\sqrt{2}}{\pi} U_{LN,RMS} = \frac{2\sqrt{2}}{\pi} \cdot 230 = 207V$$

c)

T=TILL: $V_{dc} - L \frac{\Delta \bar{i}_L}{t_T} = 0 \Rightarrow \Delta \bar{i}_L = \frac{V_{dc}}{L} t_T = \frac{V_{dc}}{L} T_{sw} \delta_T$

T=FRAN: $V_{dc} - L \left(-\frac{|\Delta \bar{i}_L|}{t_D}\right) - V_o = 0 \Rightarrow |\Delta \bar{i}_L| = \frac{-V_{dc} + V_o}{L} t_D$

Ansluten drif $\Rightarrow t_D = T_{sw} - t_T = (1 - \delta_T) T_{sw}$

LIKHET: $\frac{V_{dc}}{L} T_{sw} \delta_T = \frac{V_o - V_{dc}}{L} (1 - \delta_T) T_{sw} \Rightarrow$


$$V_{dc} \cdot \delta_T = (V_o - V_{dc})(1 - \delta_T)$$

$$V_{dc} \cdot \delta_T = V_o - V_{dc} - V_o \delta_T + V_{dc} \delta_T \Rightarrow$$

$$\delta_T = \frac{V_o - V_{dc}}{V_o} = \frac{280 - 207}{280} = 0,26$$

d)

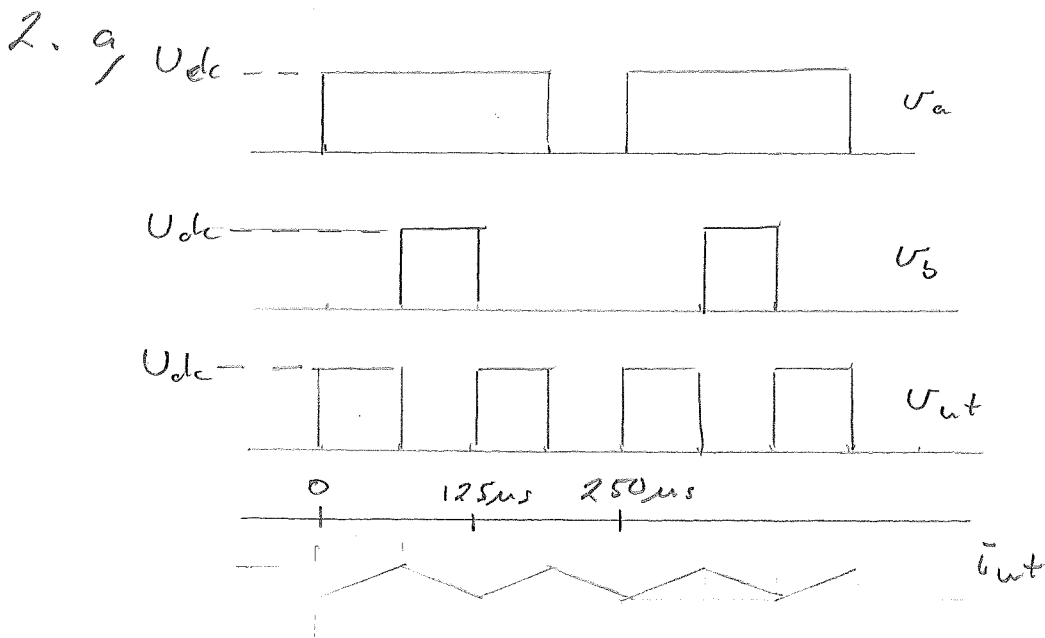T=TILL $\Rightarrow \Delta \bar{i}_L = \frac{V_{dc}}{L} \delta_T T_{sw} = \frac{207}{1,5 \cdot 10^{-3}} \cdot 0,26 \cdot \frac{1}{50 \cdot 10^3} = 0,72A$



b) IGBT

FIG 7 $\Rightarrow V_{CE(ON)} = 1,4 \text{ V}$ üd 100 A

$$P_{cond} = V_{CE(ON)} \cdot I_c \cdot \delta_i = 1,4 \cdot 100 \cdot 0,9 = 126 \text{ W}$$

FIG 4 $\Rightarrow E_{on} = 60 \text{ mWs}$ üd 600 V 300 A

$E_{off} = 40 \text{ mWs}$ — " —

$$P_{on} = 60 \cdot 10^{-3} \frac{750}{600} \cdot \frac{100}{300} \cdot 4 \text{ kHz} = 100 \text{ W}$$

$$P_{off} = 40 \cdot 10^{-3} \frac{750}{600} \cdot \frac{100}{300} \cdot 4 \text{ kHz} = 66,7 \text{ W}$$

$$P_{Loss, IGBT} = P_{on} + P_{off} + P_{cond} = 100 + 66,7 + 126 = 292,7 \text{ W}$$

FWD

FIG 10 $\Rightarrow V_D(ON) = 1,4 \text{ V}$ üd 100 A

$$P_{cond} = V_D(ON) \cdot I_D \cdot \delta_D = 1,4 \cdot 100 \cdot 0,1 = 14 \text{ W}$$

FIG 4 $\Rightarrow E_{rr} = 18 \text{ mWs}$ üd 600 V 300 A

$$P_{rr} = 18 \cdot 10^{-3} \frac{750}{600} \cdot \frac{100}{300} \cdot 4 \text{ kHz} = 30 \text{ W}$$

$$P_{Loss, FWD} = 14 + 30 = 44 \text{ W}$$

c) IGBT

$$R_{th,fs} = 0,11 + 0,038 = 0,148 \text{ } ^\circ\text{C/W}$$

$$\begin{aligned} T_{h,max,IGBT} &= T_f - R_{th,fs} \cdot P_{Loss,IGBT} = \\ &= 125 - 0,148 \cdot 292,7 = 81,7^\circ\text{C} \end{aligned}$$

FWD

$$R_{th,fs} = 0,17 + 0,038 = 0,208 \text{ } ^\circ\text{C/W}$$

$$\begin{aligned} T_{h,max,FWD} &= T_f - R_{th,fs} \cdot P_{Loss,FWD} = \\ &= 125 - 0,208 \cdot 44 = 115,8^\circ\text{C} \end{aligned}$$

IGBT Begrenser $\Rightarrow T_{h,max} = 81,7^\circ\text{C}$

$$\begin{aligned} P_{Loss,tot} &= 2 (P_{Loss,IGBT} + P_{Loss,FWD}) = \\ &= 2 (292,7 + 44) = 673,4\text{W} \end{aligned}$$

$$R_{th,ha} = \frac{T_{h,max} - T_{a,max}}{P_{Loss,tot}} = \frac{81,7 - 45}{673,4} = 0,053 \text{ } ^\circ\text{C/W}$$

$$3. a) \quad U_L = L \frac{di_L}{dt} \approx L \frac{\Delta \bar{i}}{\Delta t}$$

$$L = \frac{U_L}{\frac{\Delta \bar{i}}{\Delta t}} = \frac{100}{\frac{0,8}{8 \cdot 10^{-6}}} = 1 \text{ mH}$$

$$b) \quad T = \text{TILL: } V_{dc} - L_1 \frac{\Delta \bar{i}_1}{\Delta t} = 0 \Rightarrow \Delta \bar{i}_1 = \frac{V_{dc}}{L_1} t_T$$

$$T = \text{FRÅN: } -L_2 \frac{\Delta \bar{i}_2}{\Delta t} = V_0 \Rightarrow |\Delta \bar{i}_2| = \frac{V_0}{L_2} t_D$$

Anslutan drift

$$|\Delta \bar{i}_2| = \frac{V_0}{L_2} (T - t_T)$$

$$\Delta \bar{i}_2 = \frac{N_1}{N_2} \Delta \bar{i}_1$$

$$L_2 = \left(\frac{N_2}{N_1} \right)^2 L_1$$

$$\text{LIKHEIT: } \frac{V_{dc}}{L_1} t_T = \frac{N_2}{N_1} \left(\frac{V_0 (T - t_T)}{\left(\frac{N_2}{N_1} \right)^2 \cdot L_1} \right) =$$

$$= \frac{N_2}{N_1} \left(\frac{N_1}{N_2} \right)^2 \cdot \frac{V_0}{L_1} (T - t_T) = \frac{N_1}{N_2} \frac{V_0}{L_1} (T - t_T)$$

$$\left(V_{dc} + \frac{N_1}{N_2} \cdot V_0 \right) t_T = \frac{N_1}{N_2} V_0 \cdot T$$

$$\left(V_{dc} + \frac{N_1}{N_2} V_0 \right) \underbrace{\frac{t_T}{T}}_{\delta_T} = \frac{N_1}{N_2} V_0$$

$$V_0 = \frac{V_{dc} \delta_T}{\frac{N_1}{N_2} (1 - \delta_T)} = \frac{100 \cdot \frac{8}{20}}{5 \left(1 - \frac{8}{20} \right)} = 13,3 \text{ V}$$

$$c) \quad V_x = \frac{N_1}{N_2} \cdot V_0 = 5 \cdot 13,3 = -66,7 \text{ V}$$

$$d) \quad \text{Transistorn måste kunna blockera } V_{dc} + V_x = 100 + 66,7 = 166,7 \text{ V}$$

c, $T = FR\ddot{v}_N \Rightarrow$ Hela lastströmmen kommer från C
 V_0 faller


$$\bar{I}_C = C \frac{dV_C}{dt}$$

$$C \approx C_C \frac{\Delta t}{\Delta V_C} = \bar{I}_0 \frac{\Delta t}{\Delta V_C} = \bar{I}_0 \frac{t_T}{0,01 \cdot V_0} =$$

$$= \underbrace{\left(\frac{1,2 + 0,4}{2} \right) \frac{8}{20} \cdot 5}_{\bar{I}_0} \cdot \frac{8 \cdot 10^{-6}}{0,01 \cdot 13,3} = \underline{\underline{96 \mu F}}$$

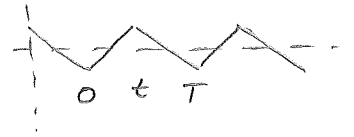4. b)

$$v = \frac{d\psi}{dt} = \frac{dBNA}{dt} \Rightarrow \frac{dB}{dt} = \frac{1}{NA}$$



$$\begin{aligned} B(t) - B(0) &= \int_0^t \frac{1}{NA} v(t) dt = \\ &= \int_0^t \frac{v}{NA} dt = \frac{v}{NA} (t - t_0) \end{aligned}$$

$$\hat{B} - (-\hat{B}) = \frac{v}{NA} \left(\frac{T}{2} - 0 \right) \Rightarrow$$

$$\hat{B} = \frac{v \cdot T}{4NA} = \frac{v}{4NAf}$$

$$= \frac{12}{4 \cdot 25 \cdot 15 \cdot 10^{-6} \cdot 10 \text{ kHz}} = 0,8 \text{ T}$$

c)


$$\begin{aligned} I_{Ldc, rms} &= \sqrt{I_{dc, rms}^2 + I_{G, rms}^2} = \\ &= \sqrt{12^2 + \left(\frac{3}{\sqrt{2}} \right)^2} = 12,2 \text{ A} \end{aligned}$$

d)

Varje diöd leder $1/3$ av grundtonperioden
Strömmen i diöden är då $i_D = i_{Ldc}$

$$\begin{aligned} I_{D, rms} &= \sqrt{\frac{1}{T} \int_T i_D^2(t) dt} = \sqrt{\frac{1}{T} \int_{T/3} i_D^2(t) dt} = \\ &= \sqrt{\frac{1}{3} \frac{1}{T/3} \int_{T/3} i_{Ldc}^2(t) dt} = \\ &= \sqrt{\frac{1}{3} \sqrt{\frac{1}{T/3} \int_{T/3} i_{Ldc}^2(t) dt}} = \\ &= \frac{1}{\sqrt{3}} \sqrt{\frac{1}{T/6} \int_{T/6} i_{Ldc}^2(t) dt} = \frac{1}{\sqrt{3}} \cdot I_{Ldc, rms} = \\ &= \frac{1}{\sqrt{3}} \cdot 12,2 = 7,04 \text{ A} \end{aligned}$$


5 a/

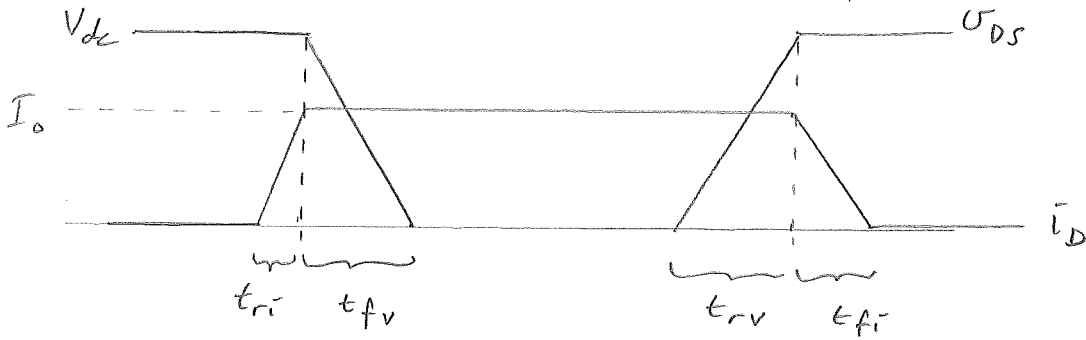

$$E_{on} = \int_0^{t_{ri}+t_{fv}} V_{DS} \cdot i_D dt = V_{dc} \cdot I_0 \cdot \frac{t_{ri}+t_{fv}}{2} = 250 \cdot 100 \cdot \frac{50n + 150n}{2} = 2,5 mJ$$

$$E_{off} = \int_0^{t_{rv}+t_{fi}} V_{DS} \cdot i_D dt = V_{dc} \cdot I_0 \cdot \frac{t_{rv}+t_{fi}}{2} = 250 \cdot 100 \cdot \frac{200n + 100n}{2} = 3,75 mJ$$

b/

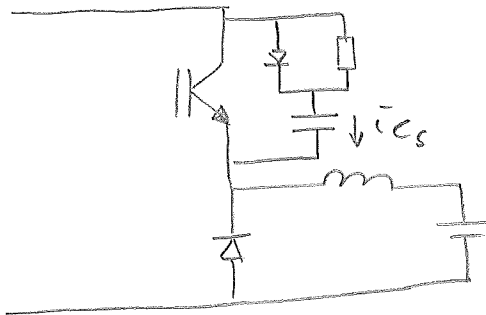

$$\bar{i}_{cs} = \frac{I_0 t}{t_{fi}} \quad 0 < t < t_{fi}$$

$$\bar{i}_{cs}(0) = 0$$

$$U_{cs} = U_{DS} = \frac{1}{C_s} \int_0^t \bar{i}_{cs} dt = \int_0^t \frac{I_0 t}{t_{fi}} dt = \frac{I_0 t^2}{2 C_s t_{fi}}$$

U_{cs} ska nå V_{dc} på tiden t_{fi}

$$C_s = \frac{I_0 t_{fi}}{2 V_{dc}} = \frac{100 \cdot 100n}{2 \cdot 250} = \underline{\underline{20 nF}}$$

$$c) \quad p(t) = v_{DS}(t) \cdot i_D(t) = v_{CS}(t) \cdot i_T(t) \quad 0 < t < t_{fr}$$

$$E_{OFF} = \int_{t_{fr}} v_{CS}(t) \cdot i_T(t) dt =$$


$$= \int_{t_{fr}} \frac{I_0 t^2}{2 C_s t_{fr}} \cdot I_0 \left(1 - \frac{t}{t_{fr}}\right) dt =$$

$$= \frac{I_0^2}{2 C_s t_{fr}} \int_0^{t_{fr}} \left(t^2 - \frac{t^3}{t_{fr}} \right) dt =$$

$$= \frac{I_0^2}{2 C_s t_{fr}} \left[\frac{t^3}{3} - \frac{t^4}{4} \right]_0^{t_{fr}} =$$

$$= \frac{I_0^2 \cdot t_{fr}^2}{24 C_s} = \frac{100^2 \cdot 100n^2}{24 \cdot 20nF} = \underline{\underline{0,21mJ}}$$

6 a/

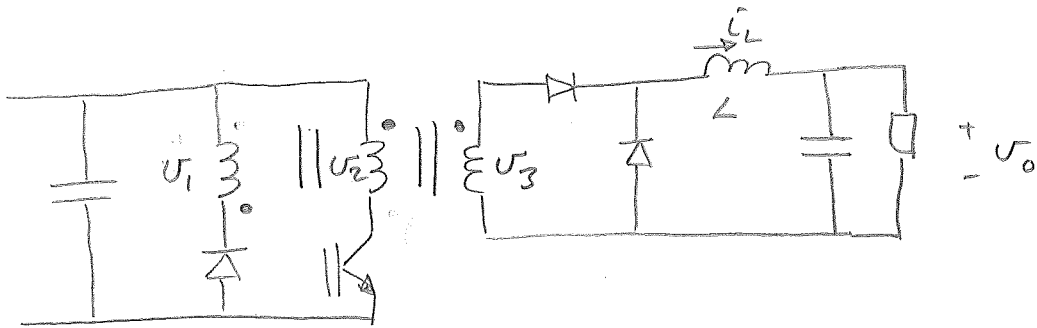

b/ T = T_{ILL}: $U_2 = V_{dc} \Rightarrow U_3 = V_{dc}$

$$V_{dc} - L \frac{di_L}{dt} - U_0 = 0 \Rightarrow V_{dc} - L \frac{\Delta i_L}{\Delta t} - U_0 = 0 \Rightarrow \Delta i_L = \frac{V_{dc} - U_0}{L} t_T$$

T = FRIÄN

$$0 - L \frac{di_L}{dt} - U_0 = 0 \Rightarrow -L \frac{|\Delta i_L|}{t_D} - U_0 = 0 \Rightarrow |\Delta i_L| = \frac{U_0}{L} t_D$$

DIÄHET: CCM $\Rightarrow t_D = (1 - \delta_T) T_{sw}$

$$\Delta i_L = |\Delta i_L| \Rightarrow$$

$$\frac{V_{dc} - U_0}{L} \delta_T T_{sw} = \frac{U_0}{L} (1 - \delta_T) T_{sw}$$

$$U_0 = \delta_T V_{dc} = 0,2 \cdot 150 = 30V$$

c/

$$\bar{I}_{0, \text{crit}} = \frac{P_{\text{crit}}}{U_0} = \frac{0,1 \cdot 80}{30} = 0,27A$$

CCM/DCM: $\bar{I}_{0, \text{crit}} = \frac{\Delta i_L}{2} \Rightarrow \Delta i_L = 2 \cdot \bar{I}_{\text{crit}} = 2 \cdot 0,27 = 0,53$

T = T_{ILL}: $\Delta i_L = \frac{V_{dc} - U_0}{L} \delta_T T_{sw} \Rightarrow L = \frac{V_{dc} - U_0}{\Delta i_L} \delta_T \frac{1}{f_{sw}} =$

$$= \frac{150 - 30}{0,53} \cdot 0,2 \frac{1}{50 \text{kHz}} = 906 \mu H$$

d/

$$R_{\text{crit}} = \frac{U_0}{I_{\text{crit}}} = \frac{30}{0,27} = 111 \Omega$$

$$e/ \quad \Delta \bar{i}_m' = \frac{V_{dc}}{L_m'} T_{sw} \delta_T = \frac{150}{2,5 \cdot 10^{-3}} \cdot \frac{1}{50 \text{kHz}} \cdot 0,2 = 0,24 \text{ A}$$

